

**VIETNAM NATIONAL UNIVERSITY
HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY**



**Digital Systems
Lab 6
Instructor: Đoàn Nọc Cẩm**

Student	Student ID
Hồ Chí Dũng	2351016
Nguyễn Viết Thi	2451165
Trần Duy Anh	2351007

Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

OBJECTIVES

- The purpose of this lab is to learn how to connect simple input (switches) and output devices (LEDs and 7-segment) to an FPGA chip and implement a circuit that uses these devices.
- Based on the processor in lab 5, design a processor which can execute both integer number and floating-point number arithmetic operations.

PREPARATION FOR LAB 6

- Finish all the lab from 1-5.
- Students have to do lab 6, then write the report of this project. The report should include all steps of your design: block diagram, waveform, RTL viewer, FSM,...
- When reporting to the instructors, you will answer random questions to prove you understand the project.

REFERENCE

1. Intel FPGA training



AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

Requirement: Connect floating-point unit (designed in lab 3) into the enhanced processor in lab5.

 


Figure 1: A reference schematic of the enhanced processor with floating point unit

 


Figure 2: Connecting the enhanced processor to a memory and output register.

Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

Instruction:

The FPU operate on 9-bit floating-point representations. There is one sign bit, four exponent bits (exponent bias is 7) and four fraction bits. Modify the FPU in lab3 and instance the module on the design.

You are required to add one new instruction which operate with floating-point number, illustrated on Figure 3.

Operation	Function performed
addf Rx, Ry	$Rx \leftarrow Rx + Ry$ (data stored in Rx, Ry is in floating-point representation)

Figure 3: New instruction performed in the processor.

Similar to **add** and **sub** instruction, it take more than one clock to complete **addf** instruction. The control unit asserts control signals needed in successive clock cycle until the instruction has completed. When the controller detect **addf** 's opcode, it activates FPU block by setting appropriate value of **AFin**, **AddSubF**, **GFin**. In this lab, there is only one opcode left for floating-point arithmetic, hence by default, the FPU execute only the addition operation (i.e AddSubF = 0). The AddSubF signal, however, still be added in the system for later extension.

The selection signal, **Gout** are converted to 2-bit signal that identifies which result is loaded to the **Bus** (Gout = 10: select AddSub output; Gout = 01: select AddSubF output).

After completing the design, compile the circuit, download it into the FPGA chip, and ensure that your program runs properly. (Students need to write some programs that verify the design correctness).



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

CODE:

//TOP MODULE:

```

module DE10 (
    input logic    CLOCK_50, // Xung clock 50MHz của mạch
    input logic [0:0] KEY,    // KEY[0] dùng làm nút bấm Resetn
    input logic [9:9] SW,     // SW[9] dùng làm công tắc Run
    output logic [8:0] LEDR    // LEDR[8:0] nối ra 9 bóng đèn LED đỏ
);

    // --- 1. KHAI BÁO DÂY NỐI NỘI BỘ ---
    logic [8:0] ADDR;
    logic [8:0] DOUT;
    logic [8:0] DIN;
    logic      W;
    logic      Done;
    logic [8:0] BusWires; // Giữ lại để debug nếu cần

    // Tín hiệu giải mã địa chỉ (Address Decoding)
    logic ram_wr_en;
    logic led_en;

    // RAM được ghi khi 2 bit địa chỉ cao nhất A8, A7 = 00 VÀ có cờ Write (W=1)
    assign ram_wr_en = ( ~(ADDR[8] | ADDR[7]) ) & W;

    // LED được cập nhật khi A8, A7 = 01 VÀ có cờ Write (W=1)
    assign led_en = ( ~(ADDR[8] | ~ADDR[7]) ) & W;

    // --- 3. CẤM CÁC THÀNH PHẦN VÀO HỆ THỐNG ---

    // A. Lõi Vi xử lý (Processor) - ĐÃ ĐỔI TÊN THÀNH lab6
    lab6 cpu (
        .DIN(DIN),
        .Resetn(KEY[0]),
        .Clock(CLOCK_50),
        .Run(SW[9]),
        .Done(Done),
        .BusWires(BusWires),
        .ADDR(ADDR),
        .DOUT(DOUT),
        .W(W)
    );

    // B. Bộ nhớ RAM (Memory 128 words x 9 bits)
    // Lưu ý: Module này KHÔNG tự có sẵn, bạn phải tạo bằng Quartus IP Catalog!
    RAM my_ram (
        .address (ADDR[6:0]), // Chỉ lấy 7 bit thấp (A6 -> A0) để quét 128 ô
        .clock   (CLOCK_50), // RAM đồng bộ dùng chung xung clock
        .data     (DOUT),     // Dữ liệu từ CPU đẩy ra chờ ghi vào RAM
        .wren     (ram_wr_en), // Cờ báo hiệu ghi vào RAM
        .q        (DIN)      // Dữ liệu RAM nhả ra để CPU đọc (lệnh hoặc data)
    );

```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```
// C. Thanh ghi LED (Output Register)
always_ff @(posedge CLOCK_50 or negedge KEY[0]) begin
    if (!KEY[0]) begin
        LEDR <= 9'b000000000; // Reset tắt hết bóng đèn
    end else if (led_en) begin
        LEDR <= DOUT;          // Chốt dữ liệu từ DOUT ra đèn LED
    end
end

endmodule

//LAB 6
//
=====
// MODULE 1: PROCESSOR
//
=====
module lab6 #(parameter n = 9) (
    input logic [8:0] DIN,
    input logic      Resetn, Clock, Run,
    output logic     Done,
    output logic [8:0] BusWires, // Giữ lại để xem waveform
    output logic [n-1:0] ADDR,
    output logic [n-1:0] DOUT,
    output logic      W
);
    // -----
    // Khai báo dây nối nội bộ
    // -----

    logic [8:0] IR;
    logic [8:0] R0, R1, R2, R3, R4, R5, R6, R7, A, G;
    logic [8:0] AddSub_Result;
    logic      IRin, DINout, Ain, Gin, AddSub;
    logic [7:0] Rin, Rout;
    logic      ADDRin, DOUTin, W_D, incr_pc;
    logic      G_not_zero;

    // FPU Signals
    logic [8:0] AF, GF;          // Thanh ghi cho FPU
    logic      AFin, GFin, AddSubF; // Tín hiệu điều khiển FPU
    logic [1:0] Gout;            // Nâng cấp Gout lên 2-bit
    logic [8:0] AddSub_Result_F;

    // -----
    // Logic phụ trợ
    // -----

    // Kiểm tra G != 0 cho lệnh mvnz
    assign G_not_zero = (G != 9'b000000000);

    // Mạch đồng bộ 2 tầng cho chân Run (Chống Metastability)
```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```

logic run_sync_1, run_sync_2;
always_ff @(posedge Clock or negedge Resetn) begin
    if (!Resetn) begin
        run_sync_1 <= 1'b0;
        run_sync_2 <= 1'b0;
    end else begin
        run_sync_1 <= Run;
        run_sync_2 <= run_sync_1;
    end
end

// Flip-flop W: Chốt cờ Write (1 bit)
always_ff @(posedge Clock or negedge Resetn) begin
    if (!Resetn)
        W <= 1'b0;
    else
        W <= W_D;
end

// -----
// Kết nối các khối (Instantiations)
// -----

// 1. Khối Điều khiển (Control Unit)
control_unit CU (
    .Clock(Clock),
    .Resetn(Resetn),
    .Run(run_sync_2),
    .IR(IR),
    .G_not_zero(G_not_zero),
    .IRin(IRin),
    .DINout(DINout),
    .Ain(Ain),
    .Gin(Gin),
    .AFin(AFin),
    .GFin(GFin),
    .Gout(Gout),
    .AddSub(AddSub),
    .AddSubF(AddSubF),
    .Done(Done),
    .Rin(Rin),
    .Rout(Rout),
    .ADDRin(ADDRin),
    .DOUTin(DOUTin),
    .W_D(W_D),
    .incr_pc(incr_pc)
);

// 2. Các thanh ghi cơ bản & Memory
regn reg_IR    (.R(DIN),      .Rin(IRin),  .Resetn(Resetn), .Clock(Clock),
.Q(IR));
regn reg_ADDR (.R(BusWires), .Rin(ADDRin), .Resetn(Resetn), .Clock(Clock),
.Q(ADDR));

```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```
    regn reg_DOUT (.R(BusWires), .Rin(DOUTin), .Resetn(Resetn), .Clock(Clock),
.Q(DOUT));

    // 3. Thanh ghi đa dụng (R0 - R6)
    regn reg_0 (.R(BusWires), .Rin(Rin[0]), .Resetn(Resetn), .Clock(Clock),
.Q(R0));
    regn reg_1 (.R(BusWires), .Rin(Rin[1]), .Resetn(Resetn), .Clock(Clock),
.Q(R1));
    regn reg_2 (.R(BusWires), .Rin(Rin[2]), .Resetn(Resetn), .Clock(Clock),
.Q(R2));
    regn reg_3 (.R(BusWires), .Rin(Rin[3]), .Resetn(Resetn), .Clock(Clock),
.Q(R3));
    regn reg_4 (.R(BusWires), .Rin(Rin[4]), .Resetn(Resetn), .Clock(Clock),
.Q(R4));
    regn reg_5 (.R(BusWires), .Rin(Rin[5]), .Resetn(Resetn), .Clock(Clock),
.Q(R5));
    regn reg_6 (.R(BusWires), .Rin(Rin[6]), .Resetn(Resetn), .Clock(Clock),
.Q(R6));

    // Program Counter (R7)
    pc_register pc_reg_7 (
        .R(BusWires),
        .R7in(Rin[7]),
        .incr_pc(incr_pc),
        .Clock(Clock),
        .Resetn(Resetn),
        .Q(R7)
    );

    // 4. Thanh ghi cho ALU & FPU
    regn reg_A (.R(BusWires), .Rin(Ain), .Resetn(Resetn), .Clock(Clock),
.Q(A));
    regn reg_G (.R(AddSub_Result), .Rin(Gin), .Resetn(Resetn), .Clock(Clock),
.Q(G));
    regn reg_AF (.R(BusWires), .Rin(AFin), .Resetn(Resetn), .Clock(Clock),
.Q(AF));
    regn reg_GF (.R(AddSub_Result_F), .Rin(GFin), .Resetn(Resetn),
.Clock(Clock), .Q(GF));

    // 5. Khối tính toán (ALU & FPU)
    alu ALU_unit (
        .A(A), .BusWires(BusWires), .AddSub(AddSub), .Result(AddSub_Result)
    );

    lab3_r FPU_unit (
        .A(AF),
        .B(BusWires),
        .S(AddSubF),
        .Result(AddSub_Result_F),
        .z(),
        .OV()
    );

    // 6. Bộ Dồn kênh (Multiplexer)
```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```

multiplexer MUX_unit (
    .R0(R0), .R1(R1), .R2(R2), .R3(R3), .R4(R4), .R5(R5), .R6(R6), .R7(R7),
    .G(G), .GF(GF), .DIN(DIN),
    .Rout(Rout), .DINout(DINout), .Gout(Gout),
    .BusWires(BusWires)
);

endmodule

//
=====
// MODULE 2: PROGRAM COUNTER (R7)
//
=====
module pc_register #(parameter n = 9) (
    input logic [n-1:0] R,
    input logic          R7in,
    input logic          incr_pc,
    input logic          Clock, Resetn,
    output logic [n-1:0] Q
);
    always_ff @(posedge Clock or negedge Resetn) begin
        if (!Resetn)
            Q <= '0;
        else if (R7in)
            Q <= R;
        else if (incr_pc)
            Q <= Q + 1'b1;
    end
endmodule

//
=====
// MODULE 3: DECODER 3-TO-8
//
=====
module dec3to8(
    input logic [2:0] W,
    input logic      En,
    output logic [7:0] Y
);
    always_comb begin
        if (En == 1'b1)
            case (W)
                3'b000: Y = 8'b00000001;
                3'b001: Y = 8'b00000010;
                3'b010: Y = 8'b00000100;
                3'b011: Y = 8'b00001000;
                3'b100: Y = 8'b00010000;
                3'b101: Y = 8'b00100000;
                3'b110: Y = 8'b01000000;
                3'b111: Y = 8'b10000000;
            endcase
        else

```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```
        Y = 8'b00000000;
    end
endmodule

//
=====
// MODULE 4: N-BIT REGISTER
//
=====
module regn #(parameter n = 9) (
    input logic [n-1:0] R,
    input logic        Rin, Clock, Resetn,
    output logic [n-1:0] Q
);
    always_ff @(posedge Clock or negedge Resetn) begin
        if (!Resetn)
            Q <= '0;
        else if (Rin)
            Q <= R;
    end
endmodule

//
=====
// MODULE 5: ALU
//
=====
module alu (
    input logic [8:0] A,
    input logic [8:0] BusWires,
    input logic        AddSub,
    output logic [8:0] Result
);
    always_comb begin
        if (AddSub)
            Result = A - BusWires;
        else
            Result = A + BusWires;
    end
endmodule

//
=====
// MODULE 6: MULTIPLEXER
//
=====
module multiplexer (
    input logic [8:0] R0, R1, R2, R3, R4, R5, R6, R7,
    input logic [8:0] G, GF, DIN,
    input logic [7:0] Rout,
    input logic        DINout,
    input logic [1:0] Gout,
    output logic [8:0] BusWires
);
```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```

always_comb begin
    BusWires = 9'b000000000; // Mặc định

    if (DINout)          BusWires = DIN;
    else if (Gout == 2'b10) BusWires = G;
    else if (Gout == 2'b01) BusWires = GF;
    else if (Rout[0])     BusWires = R0;
    else if (Rout[1])     BusWires = R1;
    else if (Rout[2])     BusWires = R2;
    else if (Rout[3])     BusWires = R3;
    else if (Rout[4])     BusWires = R4;
    else if (Rout[5])     BusWires = R5;
    else if (Rout[6])     BusWires = R6;
    else if (Rout[7])     BusWires = R7;
end
endmodule

//
=====
// MODULE 7: CONTROL UNIT (FSM)
//
=====
module control_unit (
    input logic      Clock, Resetrn, Run,
    input logic [8:0] IR,
    input logic      G_not_zero,
    output logic     IRin, DINout, Ain, Gin, GFin, AFin, AddSub, AddSubF,
    Done,
    output logic [1:0] Gout,
    output logic [7:0] Rin, Rout,
    output logic     ADDRin, DOUTin, W_D, incr_pc
);
    typedef enum logic [2:0] {T0=3'd0, T1=3'd1, T2=3'd2, T3=3'd3, T4=3'd4,
    T5=3'd5, T6=3'd6} state_t;
    state_t Tstep_Q, Tstep_D;

    // Phân rã mã lệnh
    logic [2:0] I;
    logic [7:0] Xreg, Yreg;
    assign I = IR[8:6];

    dec3to8 decX (.W(IR[5:3]), .En(1'b1), .Y(Xreg));
    dec3to8 decY (.W(IR[2:0]), .En(1'b1), .Y(Yreg));

    // FSM State Register
    always_ff @(posedge Clock, negedge Resetrn) begin
        if (!Resetrn) Tstep_Q <= T0;
        else          Tstep_Q <= Tstep_D;
    end

    // FSM Next State Logic
    always_comb begin
        case (Tstep_Q)
            T0: if (!Run) Tstep_D = T0; else Tstep_D = T1;

```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```

T1: Tstep_D = T2;
T2: Tstep_D = T3;
T3: if (Done) Tstep_D = T0; else Tstep_D = T4;
T4: if (Done) Tstep_D = T0; else Tstep_D = T5;
T5: if (Done) Tstep_D = T0; else Tstep_D = T6;
T6: Tstep_D = T0;
default: Tstep_D = T0;
endcase
end

// FSM Output Logic
always_comb begin
    // Khởi tạo mặc định
    IRin = 0; DINout = 0; Ain = 0; Gin = 0; Gout = 2'b00;
    AFin = 0; GFin = 0; AddSub = 0; AddSubF = 0;
    Rin = 8'b0; Rout = 8'b0; Done = 0;
    ADDRin = 0; DOUTin = 0; W_D = 0; incr_pc = 0;

    case (Tstep_Q)
        T0: begin
            Rout[7] = 1'b1;
            ADDRin = 1'b1;
        end
        T1: begin
            // NHẬP CHỜ RAM
        end
        T2: begin
            IRin = 1'b1;
            incr_pc = 1'b1;
        end
        T3: begin
            case (I)
                3'b000: begin Rout = Yreg; Rin = Xreg; Done = 1; end
                3'b001: begin Rout[7] = 1'b1; ADDRin = 1'b1; end
                3'b010,
                3'b011: begin Rout = Xreg; Ain = 1; end
                3'b111: begin Rout = Xreg; AFin = 1; end
                3'b100: begin Rout = Yreg; ADDRin = 1'b1; end
                3'b101: begin Rout = Yreg; ADDRin = 1'b1; end
                3'b110: begin
                    if (G_not_zero) begin
                        Rout = Yreg;
                        Rin = Xreg;
                    end
                    Done = 1;
                end
            endcase
        end
        T4: begin
            case (I)
                3'b001: ;
                3'b010: begin Rout = Yreg; Gin = 1; AddSub = 0; end
            endcase
        end
    endcase
end

```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```

        3'b011: begin Rout = Yreg; Gin = 1; AddSub = 1; end
        3'b111: begin Rout = Yreg; GFin = 1; AddSubF = 0; end
        3'b100: ;
        3'b101: begin Rout = Xreg; DOUTin = 1'b1; end
    endcase
end

T5: begin
    case (I)
        3'b001: begin DINout = 1; Rin = Xreg; incr_pc = 1; Done = 1;
end
        3'b010,
        3'b011: begin Gout = 2'b10; Rin = Xreg; Done = 1; end
        3'b111: begin Gout = 2'b01; Rin = Xreg; Done = 1; end
        3'b100: begin DINout = 1; Rin = Xreg; Done = 1; end
        3'b101: begin W_D = 1'b1; end
    endcase
end

T6: begin
    case (I)
        3'b101: begin Done = 1; end
    endcase
end
endcase
end
endmodule

```

//LAB 3

```

module lab3_r(
    input logic [8:0] A,
    input logic [8:0] B,
    input logic S,
    output logic [8:0] Result,
    output logic z,
    output logic OV
);
    //Tách làm 3 phần là sign, frac, exp
    logic sign_A;
    logic [3:0] exp_A;
    logic [3:0] frac_A;

    logic sign_B;
    logic [3:0] exp_B;
    logic [3:0] frac_B;

    assign sign_A = A[8];
    assign sign_B = B[8];
    assign exp_A = A[7:4];
    assign exp_B = B[7:4];
    assign frac_A = A[3:0];
    assign frac_B = B[3:0];

    // --- BƯỚC 2: Xử lý phép Trừ ---

```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```
// Nếu S=1 (Trừ), đảo dấu của B. Nếu S=0 (Cộng), giữ nguyên dấu của B.
logic eff_sign_B;
assign eff_sign_B = sign_B ^ S;

    logic [4:0] w_exp_diff; //Thêm 1 bit
    // logic [2:0] w_smaller_exp;
logic [3:0] w_final_exp_temp; //Thêm 1 bit
logic [3:0] w_bigger_frac;
logic [3:0] w_smaller_frac;
logic [5:0] w_shifted_frac;
logic [3:0] w_result_frac;
logic [3:0] w_result_exp; //Thêm 1 bit
logic      w_result_sign;

prelab3_tn1 u1(
    .Exp_A(exp_A),
    .Exp_B(exp_B),
    .Exp_diff(w_exp_diff),
    // .Smaller_exp(w_smaller_exp),
    .Final_exp(w_final_exp_temp)
);

prelab3_tn3 u3(
    .Fract_A(frac_A),
    .Fract_B(frac_B),
    .Exp_diff(w_exp_diff),
    .Bigger_fract(w_bigger_frac),
    .Smaller_fract(w_smaller_frac)
);

prelab3_tn2 u2 (
    .Smaller_fract(w_smaller_frac),
    // .Smaller_exp(w_smaller_exp),
    .Exp_diff(w_exp_diff),
    .Shifted_frac(w_shifted_frac)
);

// Put the + - of the S into the sign of the B
logic eff_sign;
assign eff_sign = sign_A ^ eff_sign_B;

//Extent the bigger_frac to 6 bit. to match with the shifter_frac
logic [5:0] bigger_frac_6b;
assign bigger_frac_6b = {1'b0, 1'b1, w_bigger_frac};

logic [5:0] w_Temp_fract;
assign w_Temp_fract = (eff_sign == 1'b1)? (bigger_frac_6b -
w_shifted_frac) : (bigger_frac_6b + w_shifted_frac);

prelab3_tn4 u4(
    .Temp_fract(w_Temp_fract),
    .Final_exp(w_final_exp_temp),
    .Result_fract(w_result_frac),
    .Result_exp(w_result_exp)
);
```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```
prelab3_tn5 u5(  
    .Exp_diff(w_exp_diff),  
    .Fract_A(frac_A),  
    .Fract_B(frac_B),  
    .sign_A(sign_A),  
    .sign_B(eff_sign_B),  
    .Result_sign(w_result_sign)  
);  
  
//Assign the 0 result  
assign z = (w_Temp_fract == 6'b000000) ? 1'b1: 1'b0;  
  
//Assign the overflow result  
assign OV = (w_final_exp_temp == 3'd7) || (w_final_exp_temp == 3'd6 &&  
w_Temp_fract[5] == 1'b1) ? 1'b1 : 1'b0;  
  
assign Result = (z == 1'b1) ? 8'b00000000 : {w_result_sign, w_result_exp,  
w_result_frac};  
  
endmodule  
  
module prelab3_tn1(  
    input logic [3:0] Exp_A,  
    input logic [3:0] Exp_B,  
    output logic [4:0] Exp_diff,  
    output logic [3:0] Final_exp  
);  
  
assign Exp_diff = {1'b0, Exp_A} - {1'b0, Exp_B};  
  
assign Final_exp = (Exp_diff[4] == 1'b1) ? Exp_B: Exp_A;  
  
endmodule  
  
module prelab3_tn2(  
    input logic [3:0] Smaller_fract,  
    input logic [4:0] Exp_diff,  
    output logic [5:0] Shifted_fract  
);  
//Because exp_diff can be positive or negative ==> change to positive  
  
logic [4:0] shifted_val;  
  
always_comb begin  
    shifted_val = (Exp_diff[4] == 1)? - Exp_diff: Exp_diff;  
    case (shifted_val)  
        5'd0: Shifted_fract = {1'b0, 1'b1, Smaller_fract};  
        5'd1: Shifted_fract = {2'b00, 1'b1, Smaller_fract[3:1]};  
        5'd2: Shifted_fract = {3'b000, 1'b1, Smaller_fract[3:2]};  
        5'd3: Shifted_fract = {4'b0000, 1'b1, Smaller_fract[3:3]};  
        5'd4: Shifted_fract = {5'b00000, 1'b1};  
        default: Shifted_fract = {6'b000000};  
    endcase  
end  
end
```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```
endmodule

module prelab3_tn3(
    input logic [3:0] Fract_A,
    input logic [3:0] Fract_B,
    input logic [4:0] Exp_diff,
    output logic [3:0] Bigger_fract,
    output logic [3:0] Smaller_fract
);
always_comb begin
    if (Exp_diff == 5'b0000) begin
        if (Fract_A >= Fract_B) begin
            Bigger_fract = Fract_A;
            Smaller_fract = Fract_B;
        end
        else begin
            Bigger_fract = Fract_B;
            Smaller_fract = Fract_A;
        end
    end
    else begin
        if (Exp_diff[4] == 1'b1) begin
            Bigger_fract = Fract_B;
            Smaller_fract = Fract_A;
        end
        else begin
            Bigger_fract = Fract_A;
            Smaller_fract = Fract_B;
        end
    end
end
endmodule

module prelab3_tn4 (
    input logic [5:0] Temp_fract, // 6-bit intermediate fraction
    input logic [3:0] Final_exp, // Original exponent from larger operand
    output logic [3:0] Result_fract, // 4-bit normalized fraction
    output logic [3:0] Result_exp // 4-bit normalized exponent
);

// Use a priority logic to find the leading '1'
// This structure helps RTL Viewer create a cleaner Encoder block
always_comb begin
    if (Temp_fract[5]) begin
        // CASE: Overflow (Carry-out) -> Shift right, Exponent + 1
        Result_fract = Temp_fract[4:1];
        Result_exp = Final_exp + 4'd1;
    end
    else if (Temp_fract[4]) begin
        // CASE: Already Normalized -> No shift, Exponent stays same
        Result_fract = Temp_fract[3:0];
        Result_exp = Final_exp;
    end
end
```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```
    else if (Temp_fract[3]) begin
        // CASE: Shift left 1, Exponent - 1
        Result_fract = {Temp_fract[2:0], 1'b0};
        Result_exp   = Final_exp - 4'd1;
    end
    else if (Temp_fract[2]) begin
        // CASE: Shift left 2, Exponent - 2
        Result_fract = {Temp_fract[1:0], 2'b00};
        Result_exp   = Final_exp - 4'd2;
    end
    else if (Temp_fract[1]) begin
        // CASE: Shift left 3, Exponent - 3
        Result_fract = {Temp_fract[0], 3'b000};
        Result_exp   = Final_exp - 4'd3;
    end
    else if (Temp_fract[0]) begin
        // CASE: Shift left 4, Result fraction becomes 0
        Result_fract = 4'b0000;
        Result_exp   = Final_exp - 4'd4;
    end
    else begin
        // CASE: Default/Zero -> Reset output
        Result_fract = 4'b0000;
        Result_exp   = 4'd0;
    end
end
endmodule

module prelab3_tn5(
    input logic [4:0] Exp_diff,
    input logic [3:0] Fract_A,
    input logic [3:0] Fract_B,
    input logic sign_A,
    input logic sign_B,
    output logic Result_sign
);

always_comb begin
    if (Exp_diff[4] == 1'b1) begin
        Result_sign = sign_B;
    end
    else if (Exp_diff != 5'b0000) begin
        Result_sign = sign_A;
    end
    else begin
        if (Fract_B > Fract_A) begin
            Result_sign = sign_B;
        end
        else begin
            Result_sign = sign_A;
        end
    end
end
end
```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```
endmodule

// --- Bước 1: Khởi D-Flip-Flop cơ bản (Giữ nguyên) ---
module dff_ff (
    input logic d,
    input logic clk,
    input logic rst, // Reset bất đồng bộ
    input logic en,  // Enable đồng bộ
    output logic q
);
    always_ff @(posedge clk or posedge rst) begin
        if (rst)
            q <= 1'b0;
        else if (en)
            q <= d;
    end
endmodule

// --- Bước 2: Register N-bit sử dụng vòng lặp Generate ---
module register #(parameter N = 8) (
    input logic [N-1:0] D,
    input logic          clk,
    input logic          RST,
    input logic          EN,
    output logic [N-1:0] Q
);
    // Khai báo biến genvar để chạy vòng lặp sinh phần cứng
    genvar i;
    // Khởi generate để tự động nhân bản D-Flip-Flop
    generate
        for (i = 0; i < N; i = i + 1) begin : gen_dff
            // Tạo ra N khối dff_ff, mỗi khối xử lý bit thứ i
            dff_ff dff_inst (
                .d(D[i]),
                .clk(clk),
                .rst(RST),
                .en(EN),
                .q(Q[i])
            );
        end
    endgenerate
endmodule

// RAM USING IP CATALOG

// synopsys translate_off
`timescale 1 ps / 1 ps
// synopsys translate_on
module RAM (
    address,
    clock,
```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```

data,
wren,
q);

input [6:0] address;
input clock;
input [8:0] data;
input wren;
output [8:0] q;
`ifndef ALTERA_RESERVED_QIS
// synopsys translate_off
`endif
    tri1 clock;
`ifndef ALTERA_RESERVED_QIS
// synopsys translate_on
`endif

wire [8:0] sub_wire0;
wire [8:0] q = sub_wire0[8:0];

altsyncram altsyncram_component (
    .address_a (address),
    .clock0 (clock),
    .data_a (data),
    .wren_a (wren),
    .q_a (sub_wire0),
    .aclr0 (1'b0),
    .aclr1 (1'b0),
    .address_b (1'b1),
    .addressstall_a (1'b0),
    .addressstall_b (1'b0),
    .byteena_a (1'b1),
    .byteena_b (1'b1),
    .clock1 (1'b1),
    .clocken0 (1'b1),
    .clocken1 (1'b1),
    .clocken2 (1'b1),
    .clocken3 (1'b1),
    .data_b (1'b1),
    .eccstatus (),
    .q_b (),
    .rden_a (1'b1),
    .rden_b (1'b1),
    .wren_b (1'b0));

defparam
    altsyncram_component.clock_enable_input_a = "BYPASS",
    altsyncram_component.clock_enable_output_a = "BYPASS",
    altsyncram_component.init_file = "DE10.mif",
    altsyncram_component.intended_device_family = "Cyclone V",
    altsyncram_component.lpm_hint = "ENABLE_RUNTIME_MOD=NO",
    altsyncram_component.lpm_type = "altsyncram",
    altsyncram_component.numwords_a = 128,
    altsyncram_component.operation_mode = "SINGLE_PORT",
    altsyncram_component.outdata_aclr_a = "NONE",

```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

```
altsyncram_component.outdata_reg_a = "UNREGISTERED",
altsyncram_component.power_up_uninitialized = "FALSE",
altsyncram_component.read_during_write_mode_port_a =
"NEW_DATA_NO_NBE_READ",
altsyncram_component.widthad_a = 7,
altsyncram_component.width_a = 9,
altsyncram_component.width_byteena_a = 1;

endmodule
```

MIF FILE:

```
WIDTH=9;
DEPTH=128;
```

```
ADDRESS_RADIX=HEX;
DATA_RADIX=BIN;
```

```
CONTENT BEGIN
```

```
00 : 001001000;
01 : 001111000;
02 : 001011000;
03 : 010000000;
04 : 001100000;
05 : 000000001;
06 : 001010000;
07 : 101100000;
08 : 111001010;
09 : 101001011;
0A : 001110000;
0B : 000001100;
0C : 001101000;
0D : 111111111; //change to 00000010 for waveform stimulation
0E : 001010000;
0F : 111111111; //change to 00000010 for waveform stimulation
10 : 001000000;
11 : 000010000;
12 : 011010100;
13 : 110111000;
14 : 001000000;
15 : 000001110;
16 : 011101100;
17 : 110111000;
18 : 001000000;
19 : 000001100;
1A : 011110100;
1B : 110111000;
1C : 001111000;
1D : 000000110;
[1E..7F] : 000000000;
```

```
END;
```



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

CODE TESTBENCH:

```
`timescale 1ns/1ps
module DE10_tb;
    // 1. Khai báo các tín hiệu kết nối với kit DE10
    logic          CLOCK_50;    // Xung clock 50MHz
    logic [0:0] KEY;            // KEY[0] là Resetn
    logic [9:9] SW;             // SW[9] là Run
    logic [8:0] LEDR;           // Ngõ ra hiển thị LED

    // 2. Gọi module Top-level (DUT - Device Under Test)
    DE10 dut (
        .CLOCK_50(CLOCK_50),
        .KEY(KEY),
        .SW(SW),
        .LEDR(LEDR)
    );

    // 3. Tạo xung Clock 50MHz )
    initial begin
        CLOCK_50 = 0;
        forever #10 CLOCK_50 = ~CLOCK_50;
    end

    // 4. Mô phỏng
    initial begin
        // --- Trạng thái 1: Reset hệ thống ---
        KEY[0] = 0;
        SW[9] = 0;
        #100;

        // --- Trạng thái 2: Chuẩn bị chạy ---
        KEY[0] = 1;
        #100;

        // --- Trạng thái 3: Kích hoạt Run ---
        SW[9] = 1;

        // Cấp thời gian mô phỏng 5 triệu ns.
        // Đủ để bắt kỳ file .mif nào có vòng lặp trễ nhỏ (delay = 2) chạy được
        // ~150+ vòng lặp.
        #500000;

        // Dừng mô phỏng an toàn
        $stop;
    end

    // 5. Theo dõi tín hiệu (Chỉ in ra khi LEDR thay đổi để log console không bị
    // rác)
    initial begin
        $monitor("[%0t ns] LEDR (Bin): %b | LEDR (Hex): %h", $time, LEDR, LEDR);
    end


endmodule
```




Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

RTL VIEWER:

 


CPU:


 


Laboratory 6: AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

ALU:

 


FPU:

  




Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

 

Laboratory 6:


AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

   


Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

REGISTER R7:

 


MUX:

 

Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT


CONTROL UNIT:

 

Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT


FSM:

 

Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT


RAM (IP CATALOG):

 

Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

WAVEFORM:

 

We take 1.5 - 0.5 continuously. It will stop at -16 because to align 0.5 (exponent -1) with -16.0 (exponent 4), the hardware right-shifts the 0.5's fraction by their difference of 5 positions. Because this 5-position shift exceeds your 4-bit limit, the 0.5 is pushed completely off the register to zero, leaving -16.0 stuck subtracting nothing.

Hex Value (Waveform)	Binary (S - EEEE - FFFF) – LED	Mathematical Equation	Decimal Value
070	0 0111 0000	$+1.0000_2 \times 2^{(7-7)}$	1.0
060	0 0110 0000	$+1.0000_2 \times 2^{(6-7)}$	0.5
000	0 0000 0000	<i>Special Case (Zero)</i>	0.0
160	1 0110 0000	$-1.0000_2 \times 2^{(6-7)}$	-0.5
170	1 0111 0000	$-1.0000_2 \times 2^{(7-7)}$	-1.0
178	1 0111 1000	$-1.1000_2 \times 2^{(7-7)}$	-1.5
180	1 1000 0000	$-1.0000_2 \times 2^{(8-7)}$	-2.0
184	1 1000 0100	$-1.0100_2 \times 2^{(8-7)}$	-2.5
188	1 1000 1000	$-1.1000_2 \times 2^{(8-7)}$	-3.0
18c	1 1000 1100	$-1.1100_2 \times 2^{(8-7)}$	-3.5
190	1 1001 0000	$-1.0000_2 \times 2^{(9-7)}$	-4.0
192	1 1001 0010	$-1.0010_2 \times 2^{(9-7)}$	-4.5
194	1 1001 0100	$-1.0100_2 \times 2^{(9-7)}$	-5.0



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

Hex Value (Waveform)	Binary (S - EEEE - FFFF) – LED	Mathematical Equation	Decimal Value
196	1 1001 0110	$-1.0110_2 \times 2^{(9-7)}$	-5.5
198	1 1001 1000	$-1.1000_2 \times 2^{(9-7)}$	-6.0
19a	1 1001 1010	$-1.1010_2 \times 2^{(9-7)}$	-6.5

STIMULATION: It will take 1,5 – 0.5 continuously
 $1.5 - 0.5 = 1$



$1 - 0.5 = 0.5$



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

$$0.5 - 0.5 = 0$$



$$0 - 0.5 = -0.5$$



Laboratory 6:

AN ENHANCED PROCESSOR WITH FLOATING POINT UNIT

It will minus 0.5 continuously, until -16 just like the waveform.



LINK TO THE STIMULATION VIDEO:

[https://drive.google.com/file/d/1osukKjodTKgUkE9WIVXgjY3MJ7c4g7Sw/view?usp=drive link](https://drive.google.com/file/d/1osukKjodTKgUkE9WIVXgjY3MJ7c4g7Sw/view?usp=drive_link)

